



Faculty of Engineering & Technology
Electrical & Computer Engineering Department

CIRCUITS AND ELECTRONICS LABORATORY

ENEE2103

Pre-Experiment No.3

Prepared by: Faten Sultan

ID Number: 1202750

Instructor: Dr. Mohammad Jihad Al Ju'Beh

Teaching Assistant: Eng.Bilal Ismail

Section : 3

Date: 9/4/2023

Contents

Table Of figures	3
RC Circuit	4
Time constant theoretically	4
Time Constant from Simulation:	5
RL – Circuit:	5
RL circuit after the period have been changed to $T=2 \cdot$ time constant of inductor:	6
RLC Circuit:	7
Response type:.....	7
I. Overdamped voltage Response	7
II. critically damped response	8
III. underdamped response	8
II. Response Parameters	9

Table Of figures

Figure 1 Rc Circuit	4
Figure 2 Voltage Vs Time	4
Figure 3 RL Circuit	5
Figure 4 voltage response	5
Figure 5 Current across Inductor	6
Figure 6 voltage response	6
Figure 7 current response	7
Figure 8 RLC Circuit with $R=22\text{kohm}$	7
Figure 9 Overdamped voltage response with $R=22\text{kohm}$	7
Figure 10 Critical voltage response with $R=4.47\text{kohm}$	8
Figure 11 RLC circuit with $R=600\text{ohm}$	8
Figure 12 underdamped voltage response with $R=4.47\text{kohm}$	9
Figure 13 RLC circuit with $R=750\text{ohm}$	9
Figure 14 voltage response for $R=750\text{ohm}$	9

RC Circuit

We connect the circuit with 5V peak-peak, 50Hz which result in Period "PER"= $1/f=1/50=20\text{m}$. Beside to pulse width= $0.5T=10\text{m}$.

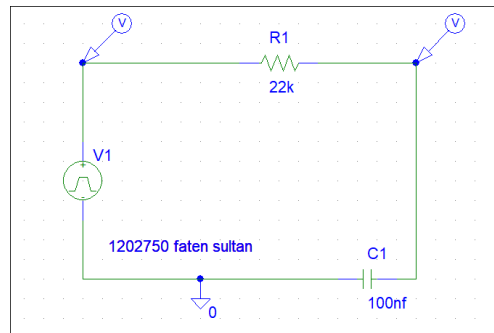


Figure 1 Rc Circuit

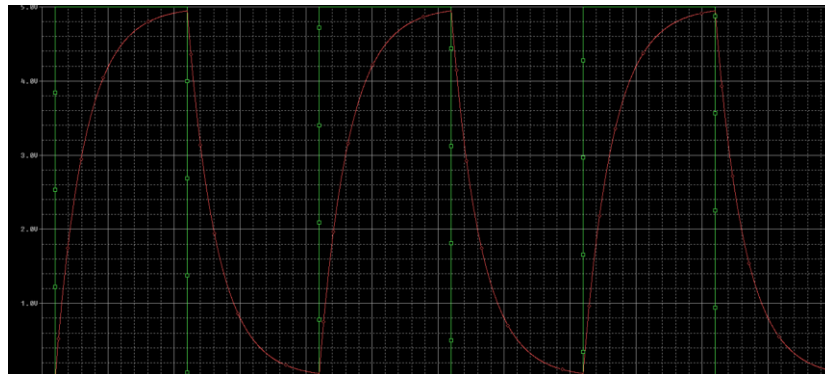


Figure 2 Voltage Vs Time

****Note that the red one is the output**

- As shown in the figure 2 simulation, **Vp Max= 4.9460V** " I used the cursor to indicate that"
- While, If we calculate **V_{charge}** using theoretical formulas:

$$V_c = V_p(1 - e^{-t/RC}) \text{ From the circuit, } R = 22\text{k}, V_p = 5\text{V}, C = 100\text{nF}, t = 0.01:$$

$$V_c = 5 * (1 - e^{-0.01/2.2*10^{-3}})$$

$$V_c = 4.9469\text{V}$$

Time constant theoretically

$$\text{As } \tau = R * C \rightarrow 22\text{k} * 100\text{n}$$

$$\tau = 2.2\text{msec}$$

Time Constant from Simulation:

As the peak voltage equals 4.9466v, and V charge = 0.63 V peak = 3.1182v at time 3.149ms, therefore the time constant that starts at the beginning is (1.0079ms) equals to $3.1459 - 1.0079 = 2.1380\text{ms}$.

We can conclude that 0.63Vm from the charging and 0.37Vm from the discharging that the time constant in simulation and time constant theoretically are approximate equal to each other

RL – Circuit:

We connect the following circuit with a square waveform 10V and a frequency=500Hz

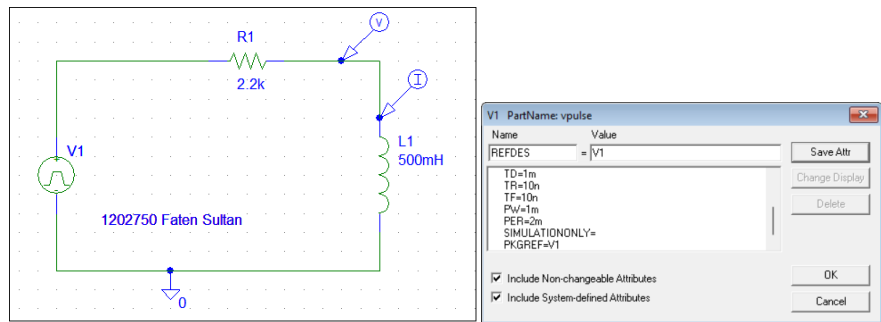


Figure 3 RL Circuit

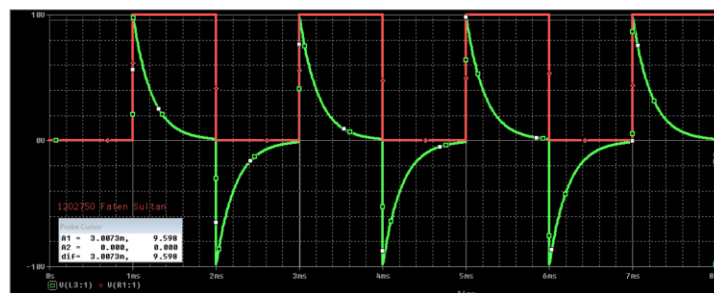


Figure 4 voltage response

The idea of connecting the circuit in figure 3 is to measure the time constant of the circuit and the steady state values of the voltage and current responses. Therefore As shown in figure 4 the steady state is 9.598v.

Now we have to repeat the steps above with Changing the period of the periodic square wave to $T=2\tau_L$

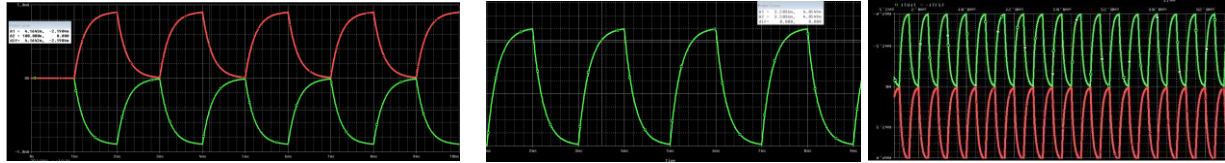


Figure 5 Current across Inductor

As Steady State of the current is when the current at each point in the circuit is constant (does not change with time). Therefore steady state is equal to 4.0549 mA .

From figure 4&5 we can conclude the following:

- $V_p = 9.598V$
- The period is $\tau = 0.22ms$ in figure 4 and the $2\tau = 0.44ms$ is the new period for figure 5
- Time Constant theoretically:
 - $\tau = L/R = 500m/2.2k \quad \tau = 0.227ms$
- Current Calculations:
 - $I_{o \text{ max}}$ from the simulation is = 4.4897mA

RL circuit after the period have been changed to $T = 2 * \text{time constant of inductor}$:

$$T = 2 * L/R = 500mH/2.2K = 0.454 \text{ ms}$$

$$F = 1/T = 2.2 \text{ kHz.}$$

Therefore $\tau = 0.22ms$, then $T = 2\tau = 0.44ms$.

$$PER = 0.44ms$$

$$PW = 0.22 \text{ ms}$$

The following figures shows the voltage and the current responses of the inductor with $T = 2\tau$.

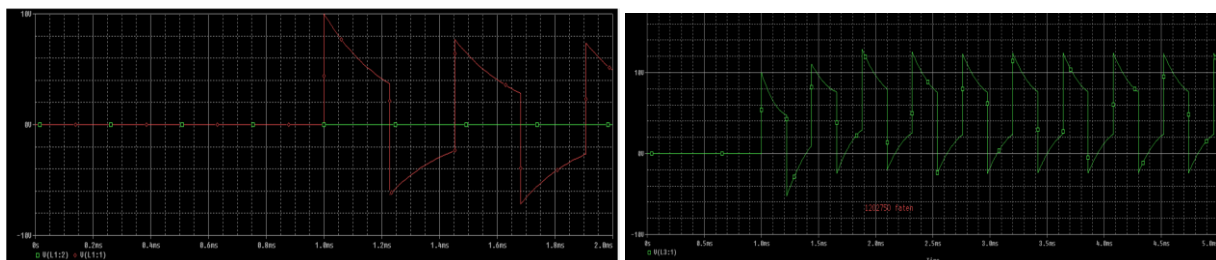


Figure 6 voltage response

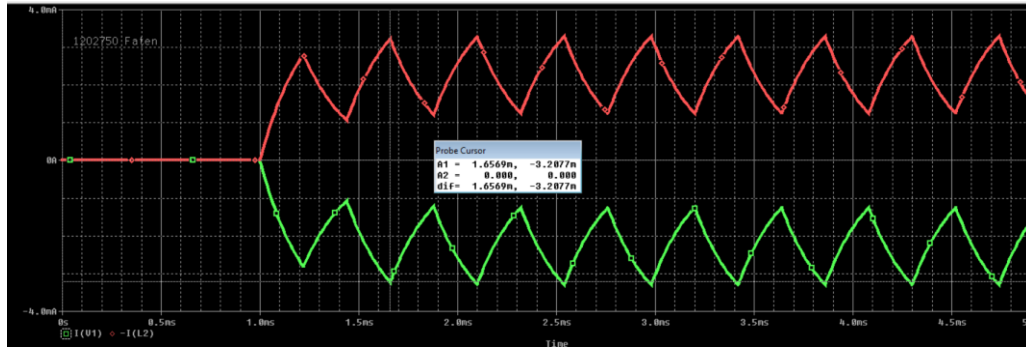


Figure 7 current response

The steady state voltage =9.915v, and the steady state current =3.207m.

RLC Circuit:

Response type:

I. Overdamped voltage Response

We connect the following circuit with $PER=period=1/f=1/30=33.33m$, $PW=$ pulse width= $0.5T=16.67m$.

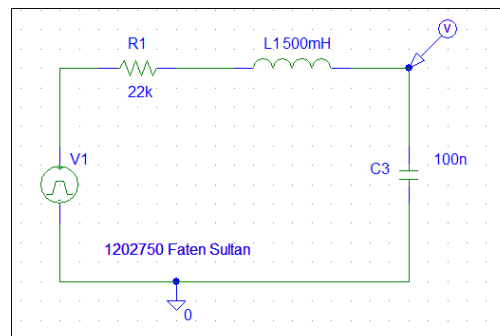


Figure 8 RLC Circuit with $R=22k\Omega$

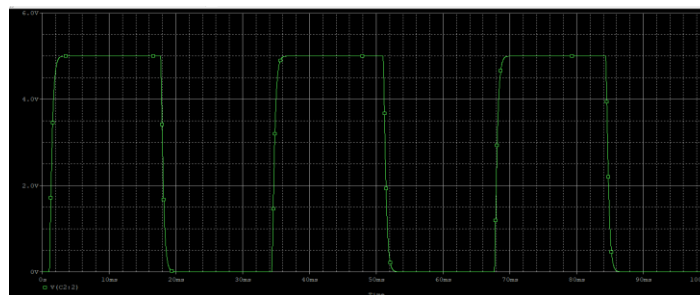


Figure 9 Overdamped voltage response with $R=22k\Omega$

II. critically damped response

Calculate R3 to give critically damped response:

Setting $\alpha = \omega_0 \rightarrow$ Critically damped response means .

the value of R of the critically damped response will be:

$$\alpha = \omega_0 \text{ where } \alpha = R/2L, \omega_0 = 1/\sqrt{LC}$$

$$R/2L = 1/\sqrt{LC}$$

$$R = 2L/\sqrt{LC}$$

$$R = 1/\sqrt{(500 \cdot 10^{-3} \cdot 100 \cdot 10^{-9})}$$

$$R = 1/\sqrt{(500 \cdot 10^{-12})}$$

$$R = 474 \text{ ohm}$$

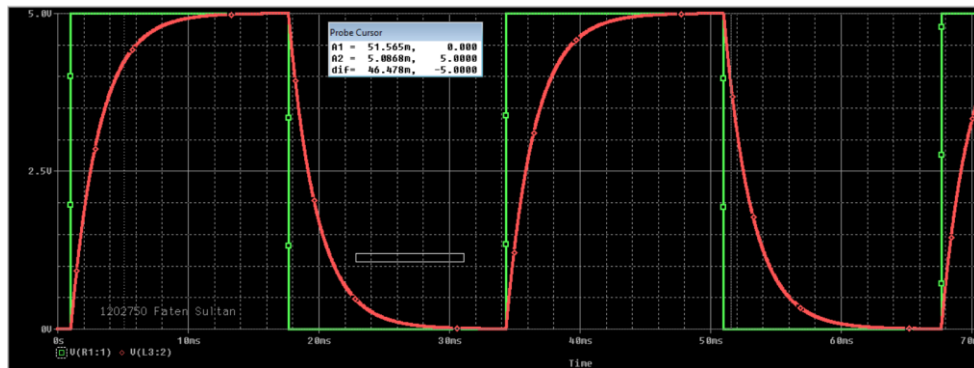


Figure 10 Critical voltage response with $R=4.47\text{kohm}$

III. underdamped response

R3 for underdamped response =600ohm

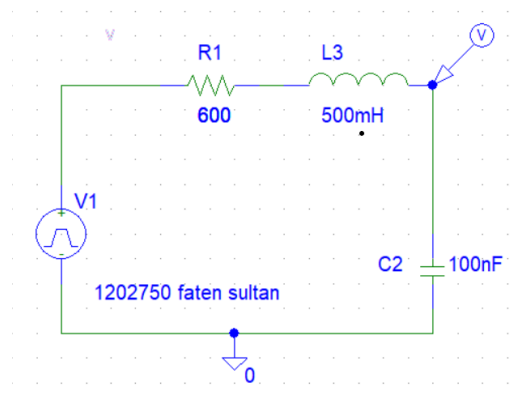


Figure 11 RLC circuit with $R=600\text{ohm}$

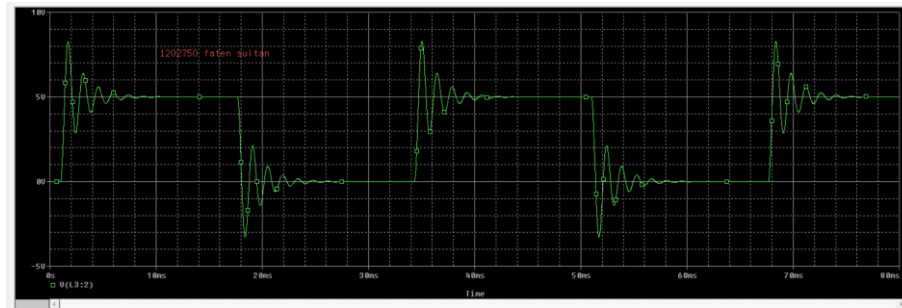


Figure 12 underdamped voltage response with $R=4.47\text{kohm}$

II. Response Parameters

R_3 is set to 750Ω , which is an underdamped response case.

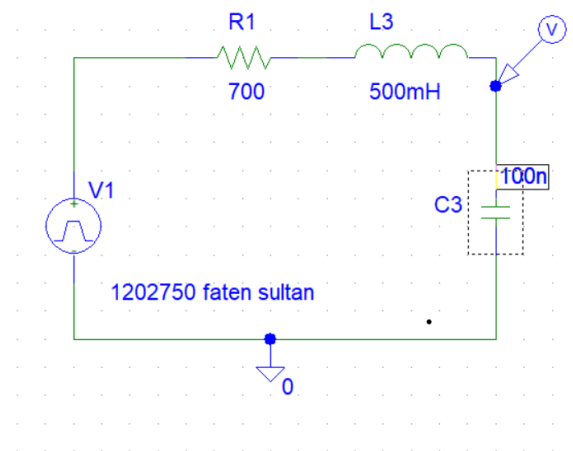


Figure 13RLC circuit with $R_3=750\text{ohm}$

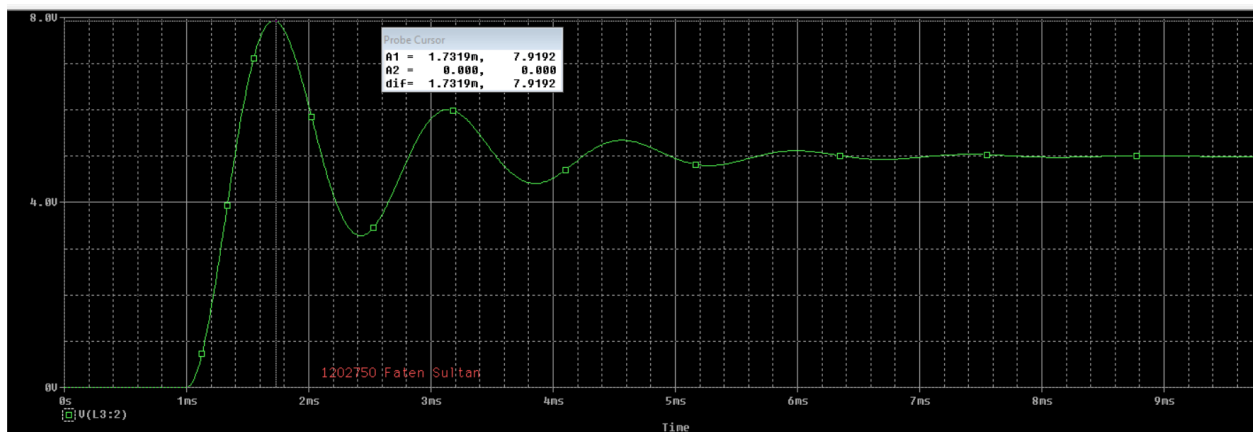


Figure 14 voltage response for $R=750\text{ohm}$

As shown in figure 14: -

$T_a = 1.71\text{ms}$, $V_a = 7.93\text{v}$, $T_b = 3.15\text{ms}$, $V_b = 6.006\text{v}$, $V_o = 5\text{v}$ ('note that these values are from the graph I have used the cursor to indicate these values')

Now we can obtain these values τ , α , ω_d .

$$\text{➤ } \tau = (T_b - T_a) / \ln ((V_a - V_o) \div (V_b - V_o)) = 1.321\text{ms}$$

$$\text{➤ } \alpha = 1/\tau$$

$$= 1/1.321 = 757 \text{ (1/sec)}$$

$$\text{➤ } \omega_d = 2\pi \div (t_b - t_a)$$

$$= 4.4278 \text{ KHz}$$

At the end we can conclude the following:

Critical Damping $\rightarrow R_3 = 4.742\text{k}\Omega$ as shown in figure 10, underdamped $\rightarrow R_3 = 600\Omega$ as shown in figure 12, overdamped $\rightarrow 22\text{k}\Omega$ as shown previously in figure 9

In addition to that our theoretical values matches with our experimental values.