



**BIRZEIT UNIVERSITY**

**Faculty of Engineering and Technology**

**Electrical and Computer Engineering Department**

**ENEE2103**

**Circuits and Electronics Lab**

**Experiment No.7**

**BJT Transistor As An Amplifier, CE, CC, CB Connection**

---

**Prepared By: Faten Sultan      ID: 1202750**

**Instructor's Name: Dr.Mohammad Jehad Al Ju'Beh.**

**Teaching assistant: Eng.Bilal Ismail.**

**Section: 2**

**May 20, 2023**

## Contents

Table Of Figures .....	3
Part one: COMMON EMITTER TRANSISTOR AMPLIFIER.....	4
Set output amplitude zero and frequency to one.....	4
Measuring $V_c$ , $V_{BE}$ , $V_{CE}$ , $I_c$ , $I_B$ :.....	5
Change the voltage input peak to obtain $V_{out} = 4V$ .....	7
Voltage Gain .....	7
Remove the 100k resistor and see calculating voltage gain.....	8
Part two: COMMON COLLECTER TRANSISTOR (AMPLIFIER): .....	8
Set the circuit as shown below .....	9
Measuring $V_c$ , $V_{BE}$ , $V_{CE}$ , $I_c$ , $I_B$ :.....	9
Perform Bias Point .....	9

## Table Of Figures

Figure 1:COMMON EMITTER TRANSISTOR AMPLIFIER.1.....	4
Figure 2:vout for the first part.....	4
Figure 3: COMMON EMITTER TRANSISTOR AMPLIFIER.2.....	5
Figure 4: simulate for COMMON EMITTER TRANSISTOR AMPLIFIER.2 .....	5
Figure 5: COMMON EMITTER TRANSISTOR AMPLIFIER 3.....	6
Figure 6:Vout with changing the voltage markers.....	6
Figure 7: Adjust amplitude of $V_i(t)$ .....	6
Figure 8: $V_o$ when $V_i(t) = 1V$ .....	6
Figure 9: $V_o$ when $V_i(t) = 1V$ with curcor measuring.....	7
Figure 10:output peak = 4V .....	7
Figure 11:rms $V(t)_o$ / rms $V(t)_b$ .....	7
Figure 12: Remove the 100k resistor .....	8
Figure 13:Gain when $R = 100k$ is removed. ....	8
Figure 14:CCT amplifier.....	9
Figure 15: When $v(t)_{op-p}=2v$ . ....	9
Figure 16: Voltage gain on 1v input in CC circuit.....	10
Figure 17:required vin to get vout peak 2v .....	10
Figure 18:Current rms for input and output.....	11
Figure 19:the output voltage and current .....	11
Figure 20:rms values for 100k resistor .....	12
Table 1 Quantity & Measured Values.....	12

## Part one: COMMON EMITTER TRANSISTOR AMPLIFIER.

### Set output amplitude zero and frequency to one

We are going to use in this part the Pot as shown below. To know to which direction the arrow will be directed, we will set  $dc = 0$  and we will simulate it in pspice if the set in pot equal to zero then the arrow is directed to the ground else it will be directed to between the two resistors.

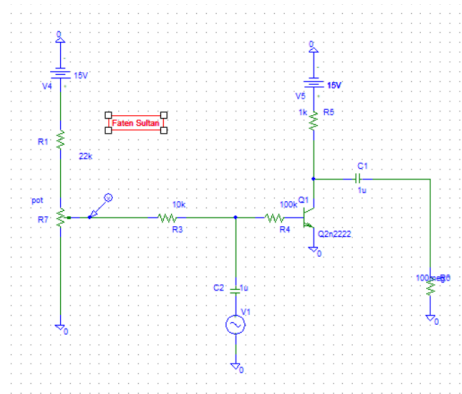


Figure 1:COMMON EMITTER TRANSISTOR AMPLIFIER.1

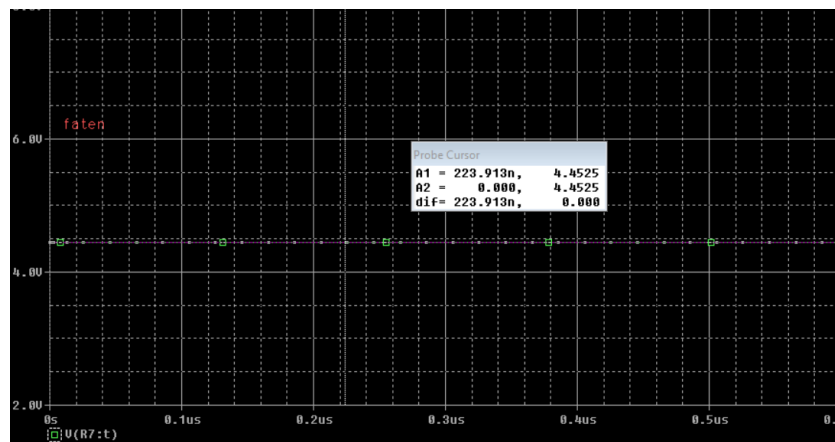


Figure 2:vout for the first part.

Since the set is equal to 4 “greater than zero “the arrow will be directed to between the two resistors and by this it will allow the voltage to be passed to the circuit

$$V_{out}=4.4525V$$

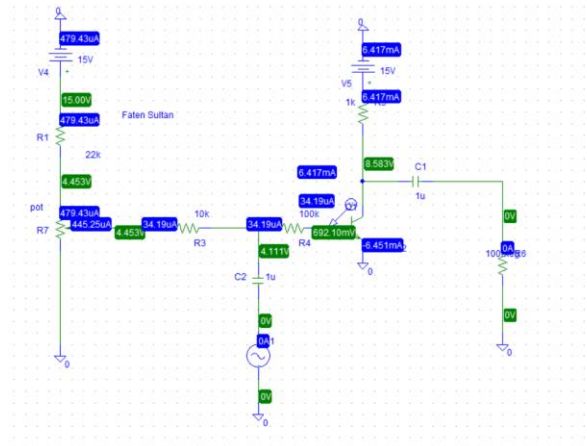


Figure 3: COMMON EMITTER TRANSISTOR AMPLIFIER.2

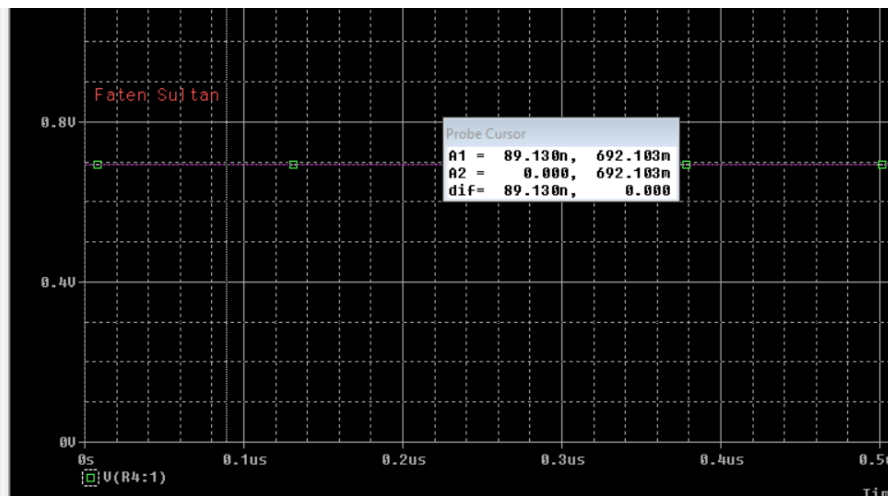


Figure 4: simulate for COMMON EMITTER TRANSISTOR AMPLIFIER.2

### Measuring $V_c$ , $V_{BE}$ , $V_{CE}$ , $I_c$ , $I_B$ :

- $V_c = 8.583 \text{ v}$
- $V_{BE} = 692.103 \text{ mv}$
- $V_{CE} = V_c - V_E = 8.583 - 0 = 8.583 \text{ v}$
- $I_c = 6.417 \text{ mA}$
- $I_B = 34.19 \text{ uA}$

**Note:**  $V_{ce} = V_c$  and  $V_{be} = V_b$  since  $V_e = 0 \text{ V}$

Now , If we put the Voltage marker in these position we will get the following simulation

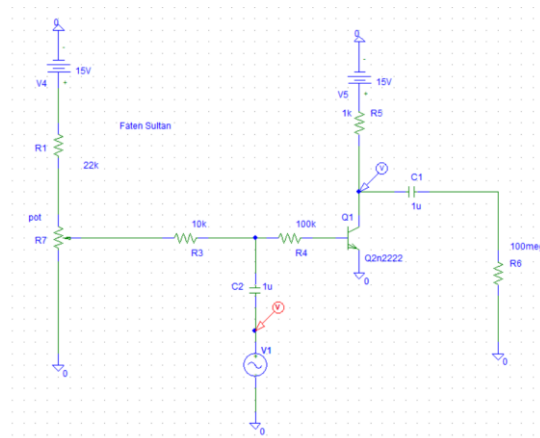


Figure 5: COMMON EMITTER TRANSISTOR AMPLIFIER 3

The result output will be:

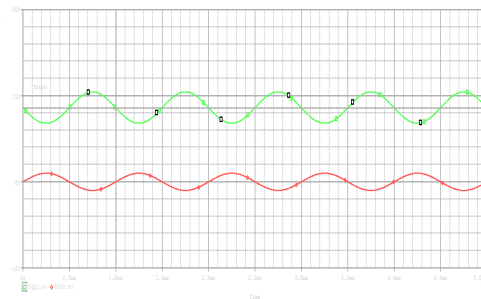


Figure 6: Vout with changing the voltage markers

The Vout is resulted from a phase shift from the input Green graph equals to 8.5825V and that is the same as dc value as a result we change the voltage detector to:

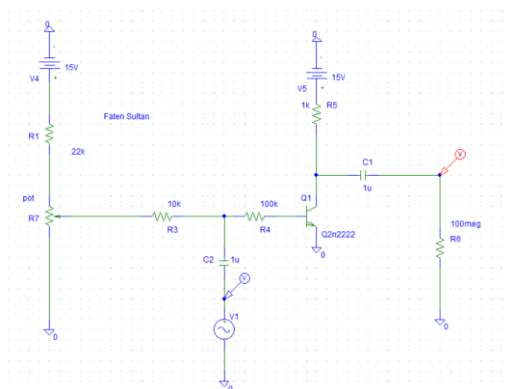


Figure 7: Adjust amplitude of  $V_i(t)$

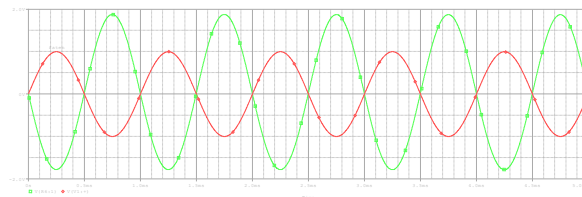


Figure 8:  $V_o$  when  $V_i(t) = 1V$

This circuit is common emitter that caused a phase shift by 180 degree.  
To calculate voltage gain we used the cursors:

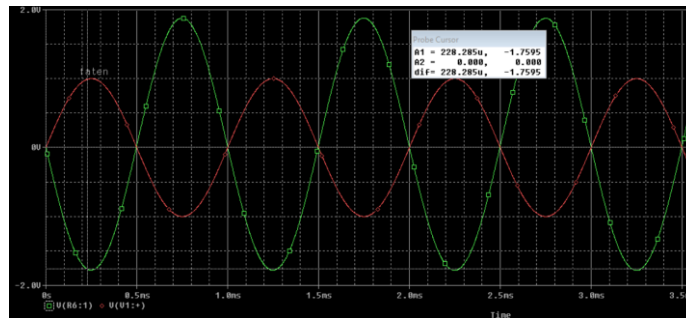


Figure 9:  $V_o$  when  $V_i(t) = 1V$  with cursor measuring

### Change the voltage input peak to obtain $V_{out} = 4V$

We want to change the voltage input peak to obtain  $V_{out} = 4V$ .

So when  $V_{amp1} = 1$  gives me 1.77595 then  $4/1.77595 = 2.273$  we set  $V_{amp1}$  in  $V_{in}$  to 2.273V and we obtain the following:

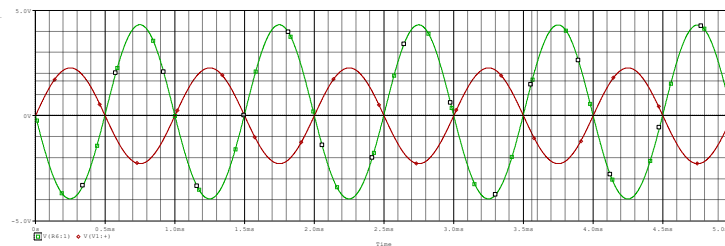


Figure 10: output peak = 4V

### Voltage Gain

Voltage gain = 1.7595V as  $V_o(t) / V_i(y) = \frac{4}{2.273}$

We use VRMs to make it easier to find gain

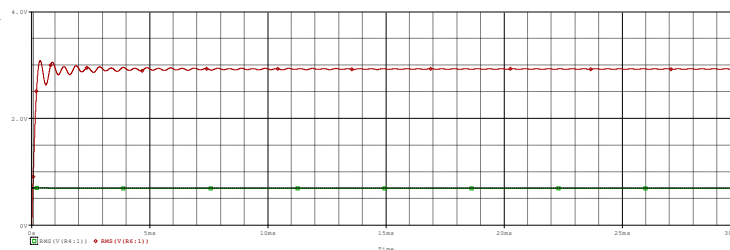


Figure 11:  $\text{rms } V(t)_o / \text{rms } V(t)_i$

$$A_v (\text{experimentally}) = \text{rms } V(t)_o / \text{rms } V(t)_i = 2.88/688.63 = 0.0041 \text{ v}$$

### Remove the 100k resistor and see calculating voltage gain

We remove the resistor that exist before BJT and the simulation was as shown below:

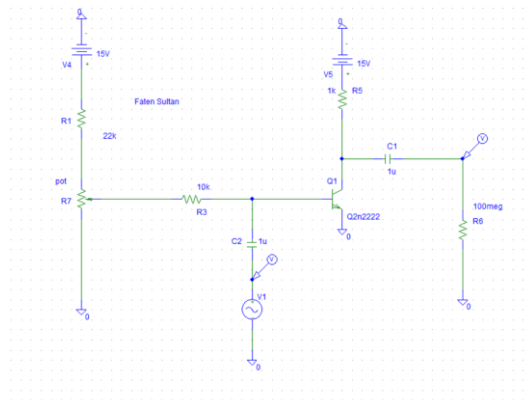


Figure 12: Remove the 100k resistor

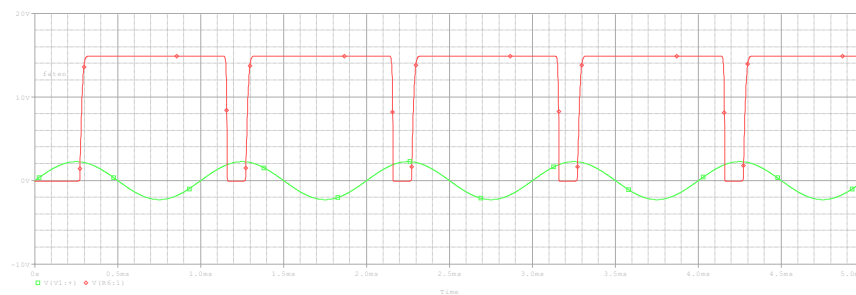


Figure 13: Gain when  $R = 100k$  is removed.

The reason the graph is looking like this is that the circuit is no longer act as amplifier, instead BJT is in either cut off region or in saturation region in other words the transistor act as a switch.

\*\*\*\*\*

### Part two: COMMON COLLECTOR TRANSISTOR (AMPLIFIER):

Here we don't have phase shift.

We connect a resistor with 100meg to represent the circuit as an open circuit



Set the circuit as shown below

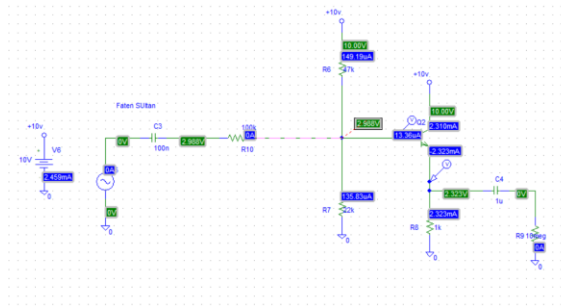


Figure 14: CCT amplifier.

Measuring  $V_c$ ,  $V_{BE}$ ,  $V_{CE}$ ,  $I_c$ ,  $I_B$ :

$$V_b = 2.988$$

$$V_{be} = 2.988 - 2.323 = 0.7$$

$$V_c = 10V$$

$$I_b = 13\mu A$$

$$I_c = 2.3mA$$

Perform Bias Point

To obtain a voltage output = 2V

We set amplitude for voltage input to 1 and we realized that the voltage gain is 0.116728

Then to obtain 2V  $\rightarrow 2/0.117 = 17$

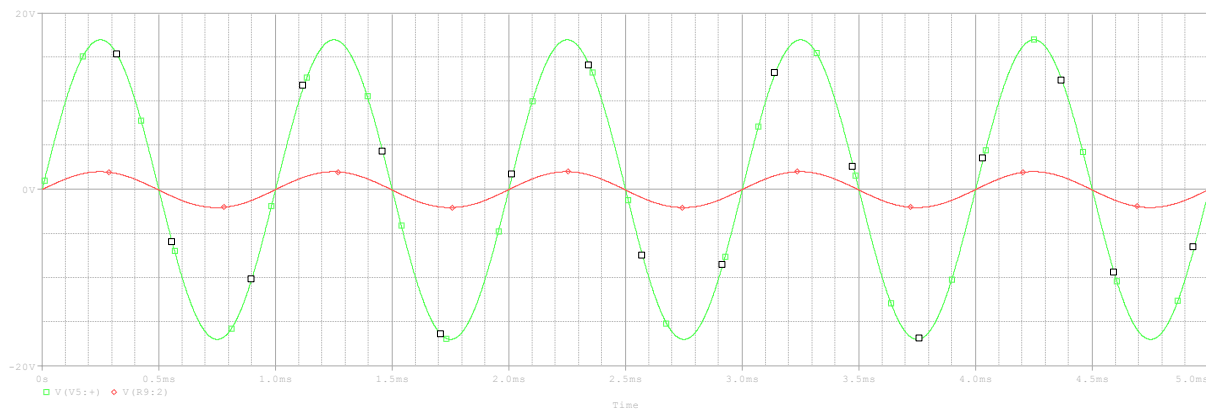


Figure 15: When  $v(t)_{op-p} = 2v$ .

To find the amplitude of the input voltage, the voltage gain must be found. The voltage gain is found by setting the amplitude of input voltage to 1 V and measuring the output.

$V_i(t)$  and  $V_o(t)$ :

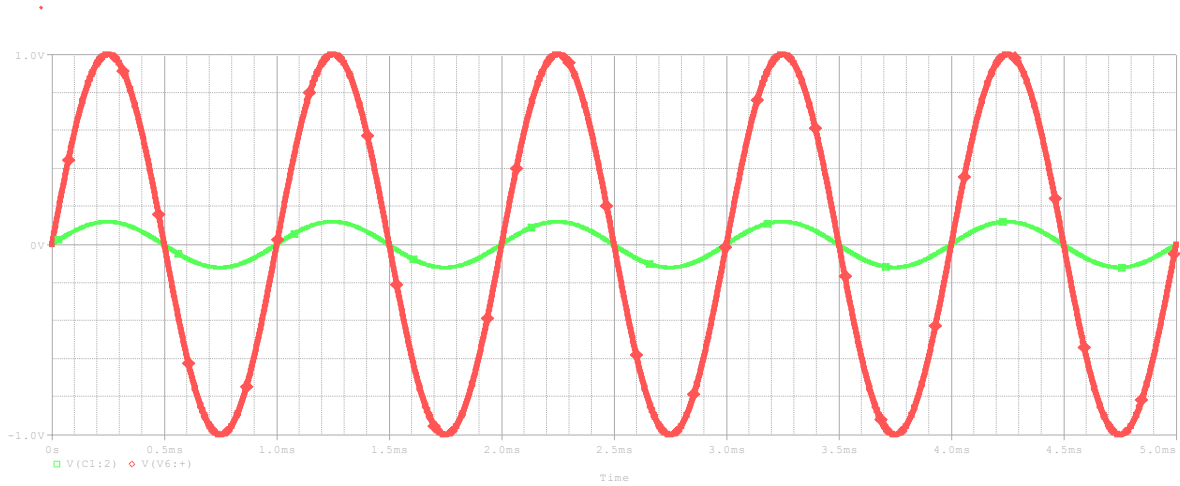


Figure 16: Voltage gain on 1v input in CC circuit

The voltage gain  $A_v$ :

$$A_v = \frac{V_o}{V_i} = \frac{0.119236}{0.9998} = 0.11926$$

Since the output is 2 V peak-peak, then the amplitude is 1 V.

$$V_i = \frac{V_o}{A_v} = \frac{1}{0.11926} = 8.385 \text{ v}$$

$V_i(t)$  and  $V_o(t)$  and  $A_v$ :

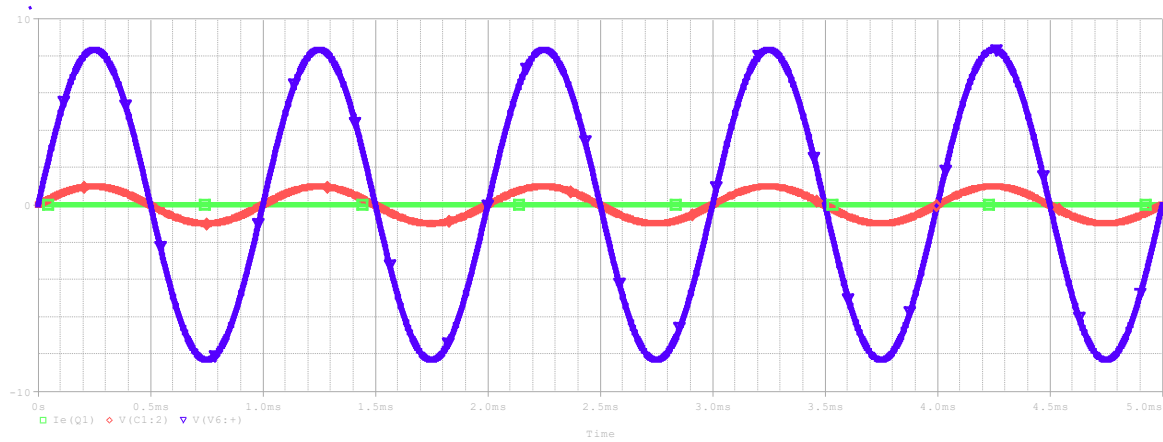


Figure 17: required vin to get vout peak 2v

$I_i(t)$  and  $I_o(t)$  and  $A_i$ :

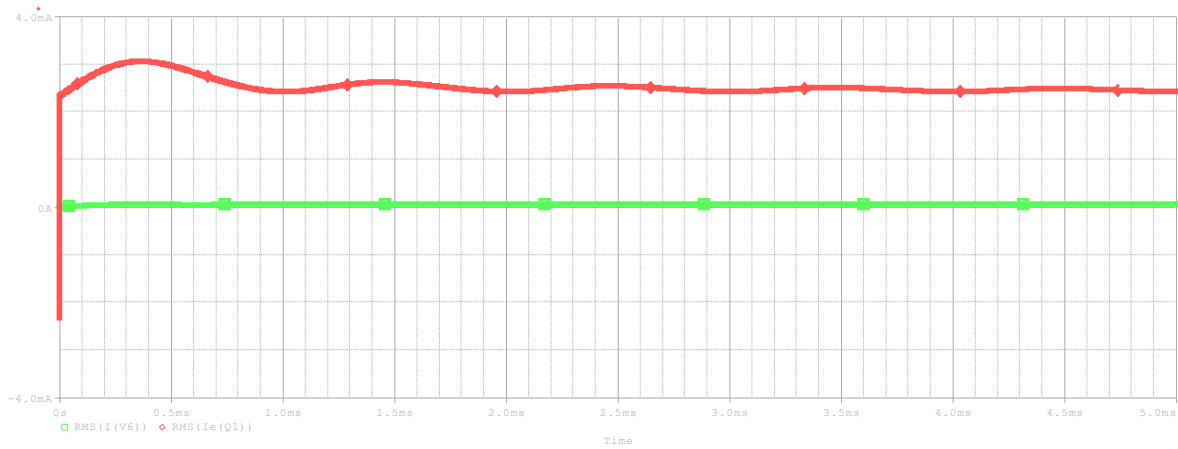


Figure 18: Current rms for input and output

The current gain  $A_i$ :

$$A_i = \frac{I_o}{I_i} = \frac{101.858 \cdot 10^{-9}}{74.560 \cdot 10^{-6}} = 1.36612 \cdot 10^{-3}$$

The input impedance  $Z_i$ :

$$Z_i = \frac{V_i}{I_i} = \frac{8.3837}{74.56 \cdot 10^{-6}} = 112442.328326 \Omega$$

$V_t(t)$  and  $I_t(t)$ :

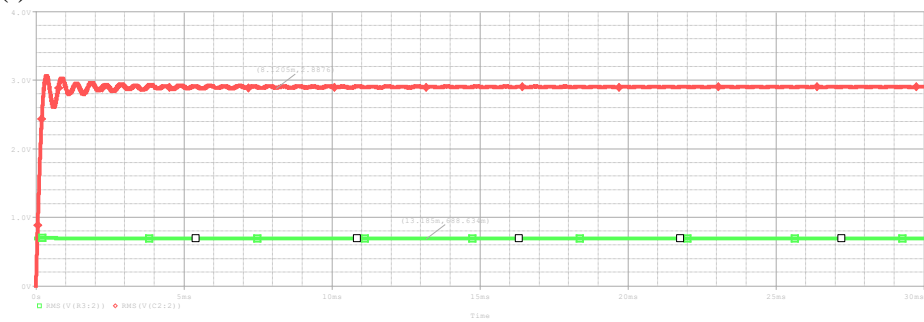


Figure 19: the output voltage and current

The output impedance  $Z_o$ :

$$Z_o = \frac{V_o}{I_o} = \frac{8.3832}{43.336 \cdot 10^{-3}} = 193.4465 \Omega$$

$V_{100k\_RMS}(t)$ :

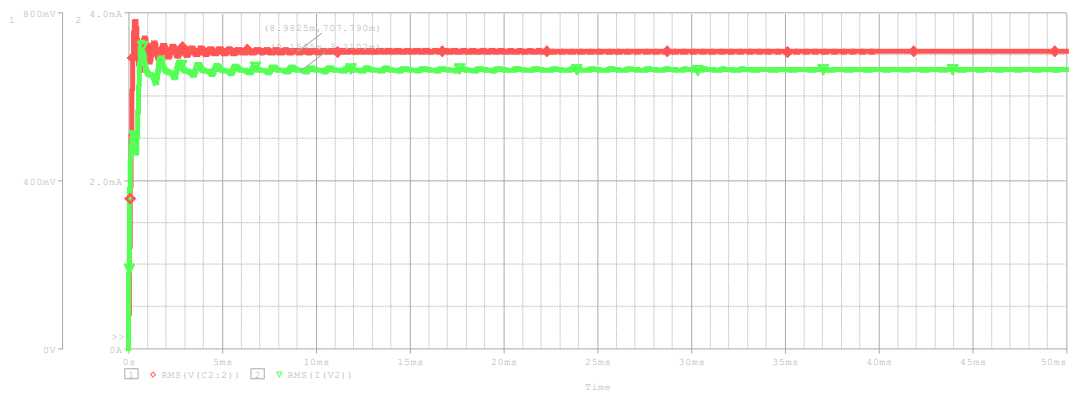


Figure 20:rms values for 100k resistor

Table 1 Quantity & Measured Values

Quantity	Measured values
$V_{in}$	8.3837 v
$V_{out}$	1.0009 v
$V_{100k\_RMS}$	7.2891 v
$i_{out}$	101.858 nA
Calculated values	
$A_v = V_{out}/V_{in}$	0.119386
$i_{in} = V_{100k\_RMS} / 100k$	72.891 uA
$A_i = i_{out}/i_{in}$	$1.3974 * 10^{-3}$
$Z_{in} = V_{in}/i_{in}$	115016.9431 $\Omega$
$Z_{out} = V_T/i_T$	193.4465 $\Omega$